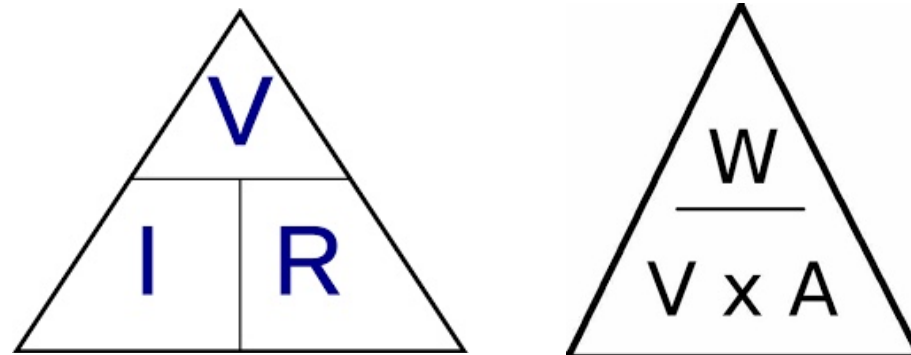


Electricity Basics


Class 2 for Gallup Solar Team 7



Electricity is the movement of electrons.
Moving electrons create charge to run your
fridge, TV, turn on lights and charge devices.

The movement of electrons can be defined
in terms that make it possible
to manage electricity.


Defining terms

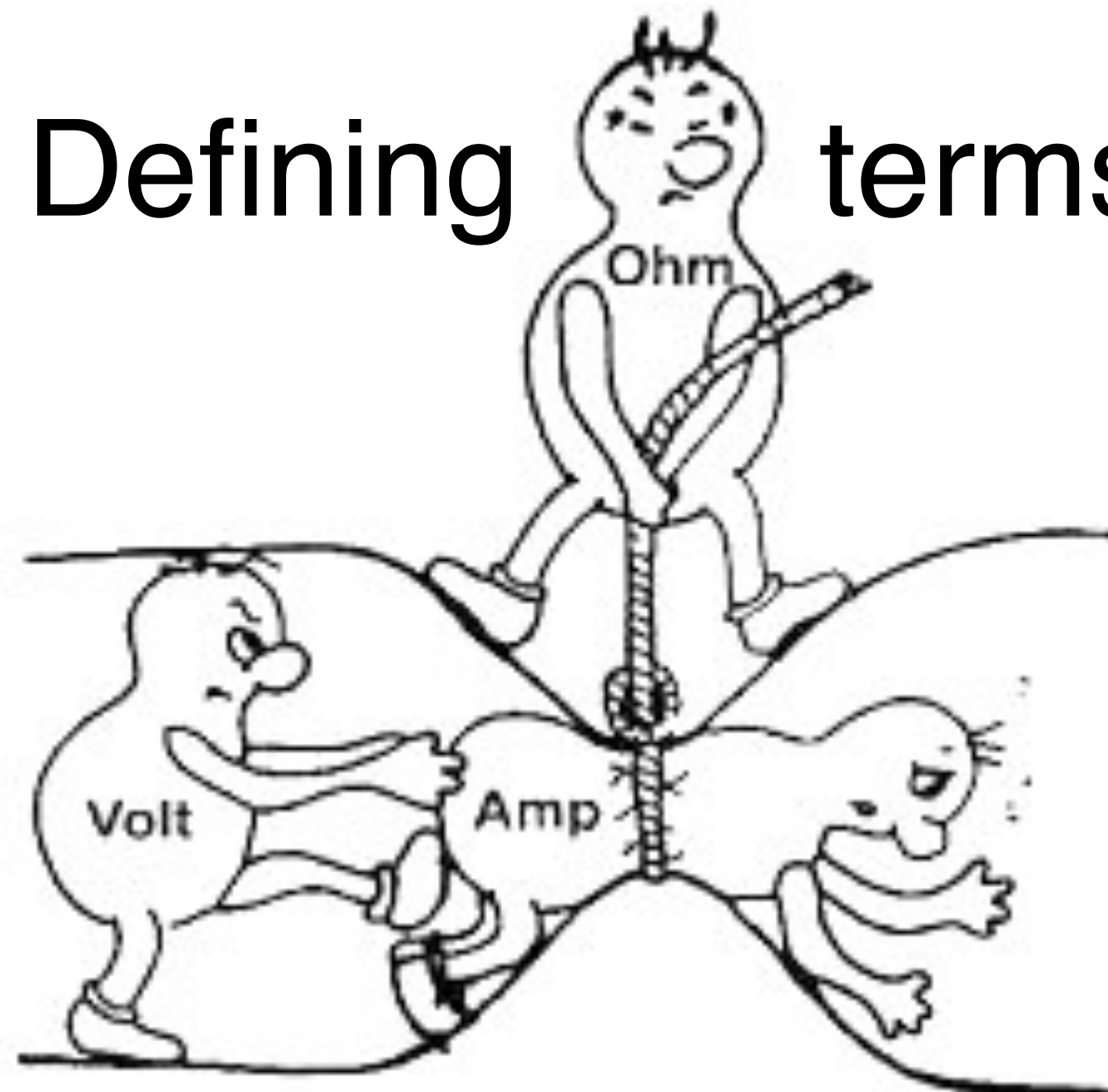

Volts Amps Ohms


*Remember forever: Amps A are the same as Current I
and Ohms Ω are the same as Resistance R*

Ohm's Law $V=IR$

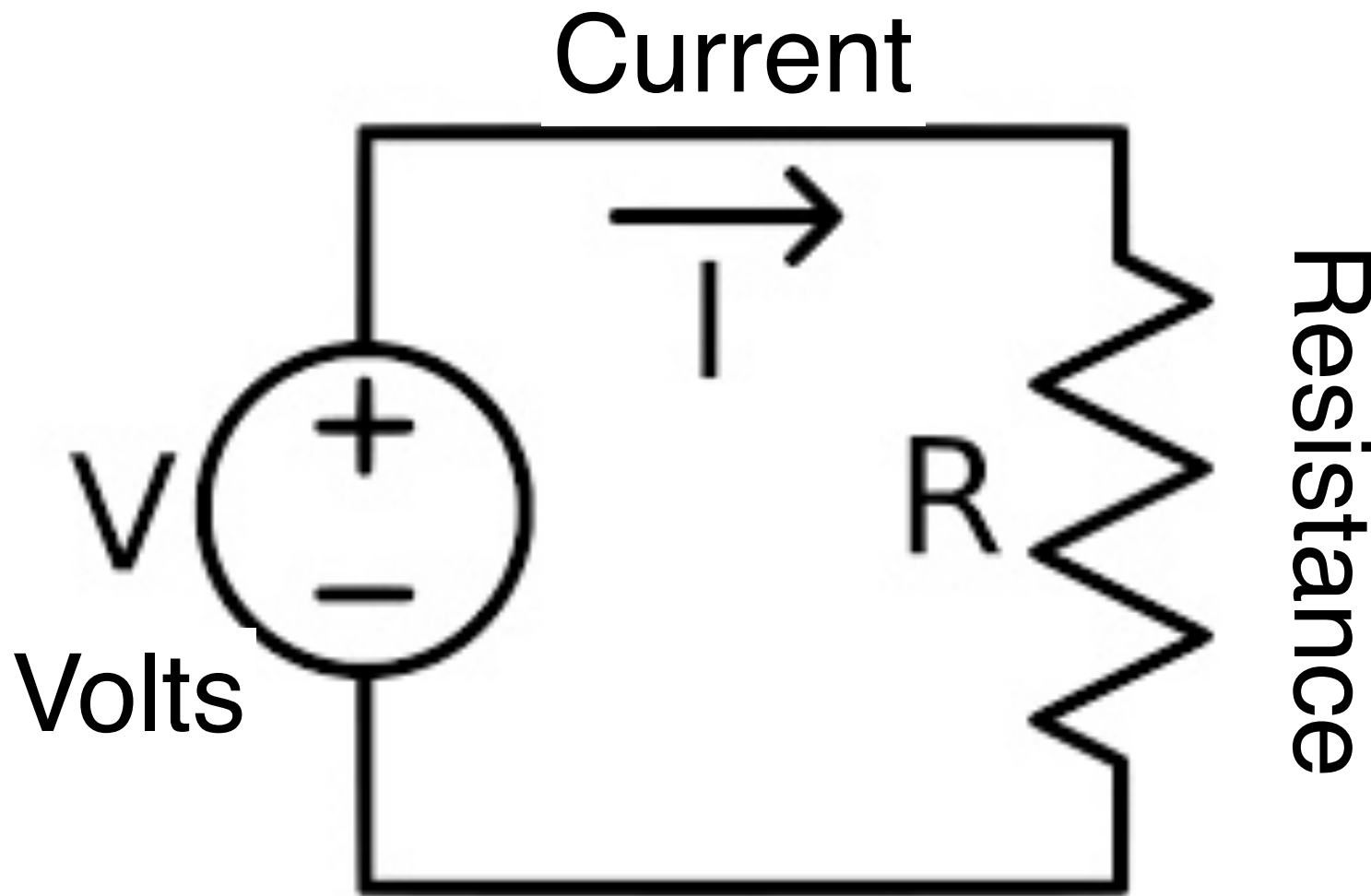


Ohm's Law defines the relationship and balance of forces between Voltage, Current and Resistance in every electric circuit.



Volts

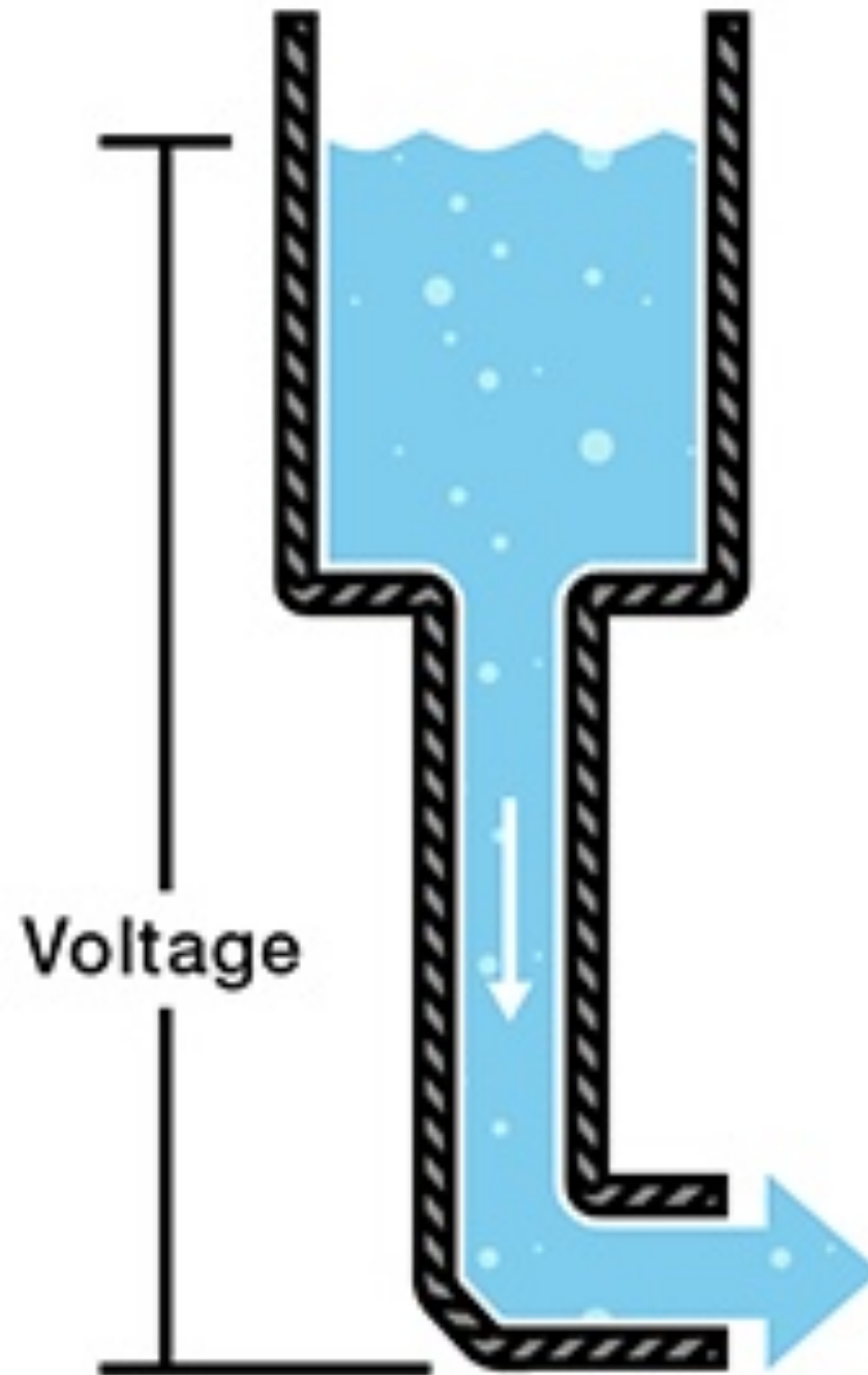


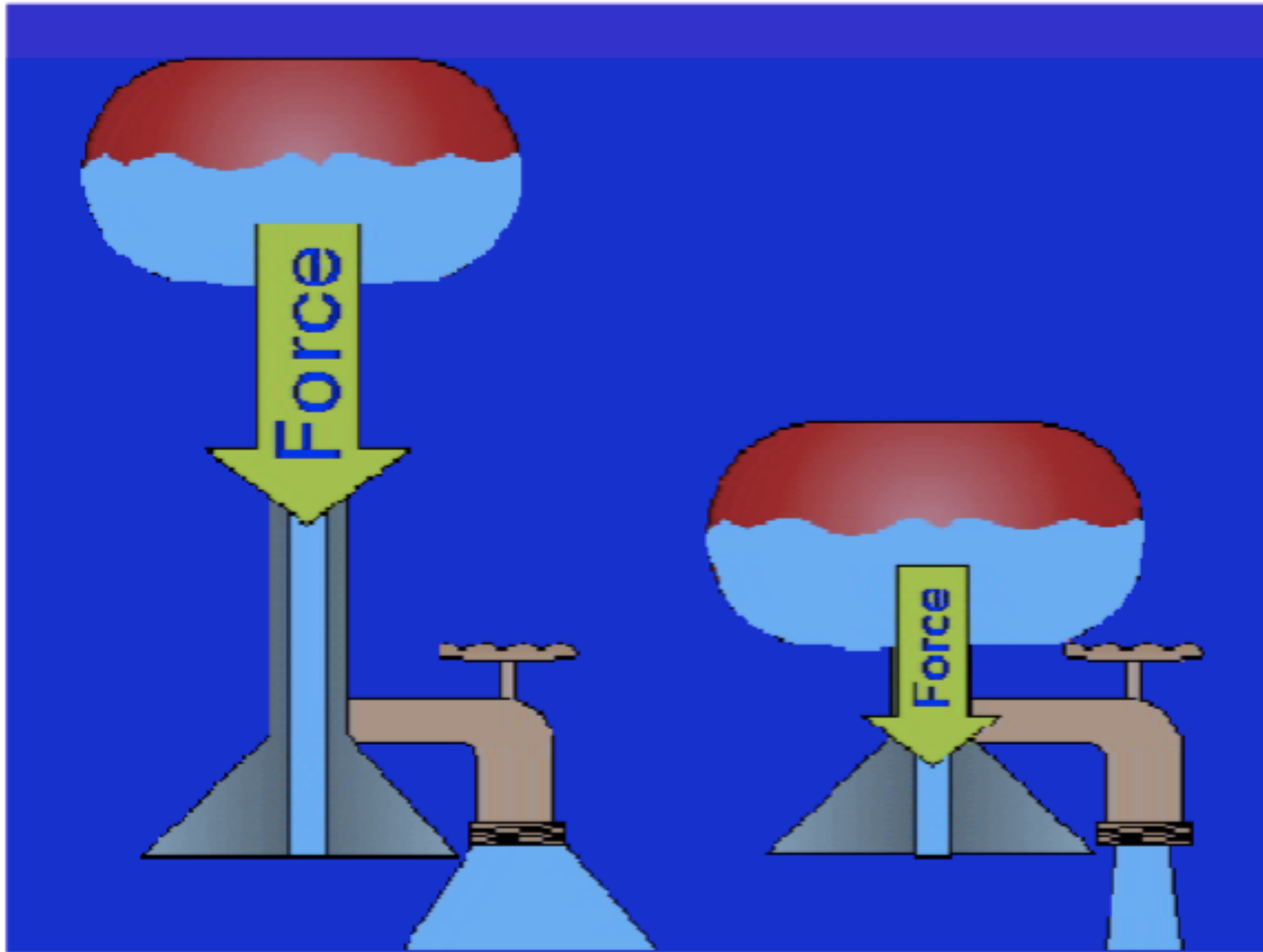
Voltage (V) is the potential charge between two points.



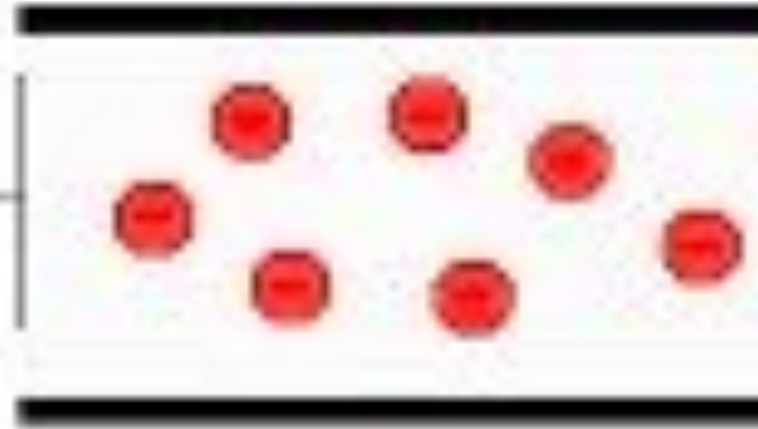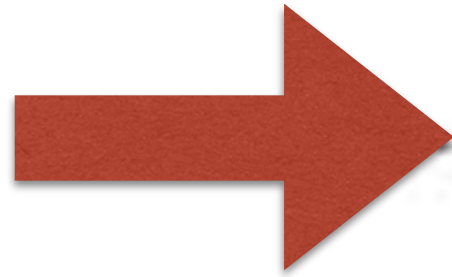Voltage is often compared to water pressure



Low Voltage = low pressure on electrons

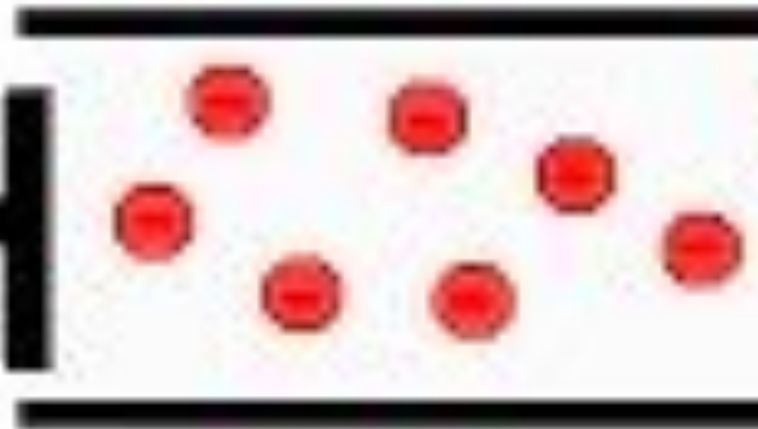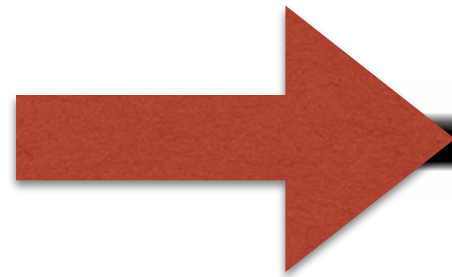

High Voltage = high pressure on electrons

Some Common Voltages

One solar cell any size **.3 -.5V**

Single-cell, rechargeable battery **1.2V**

Single-cell, non-rechargeable battery **1.5V–1.56V**

USB **5V**

Automobile battery **2.1V per cell**

Electric vehicle battery **400V**

Off-Grid Hogan System **12V or 24V**

Household outlet (Japan) **100V**

Household outlet (North America) **120V**


Household outlet (Europe, Asia, Africa, Australia) **230V**

Rapid transit third rail **600V–750V**


High-voltage electric power lines **110,000V**

Lightning **100,000,000V**

Amps Current

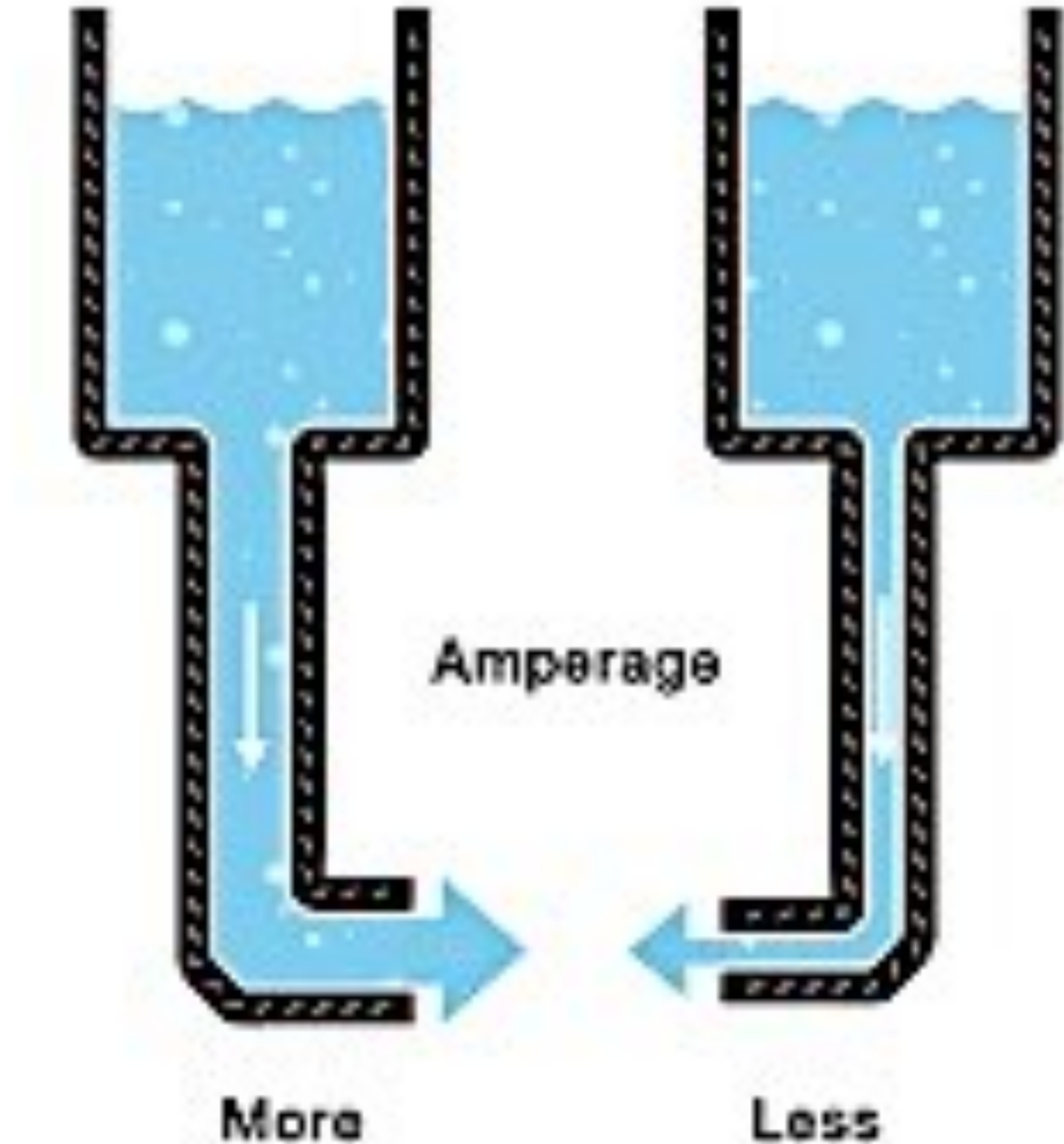


The rate at which charge is flowing.

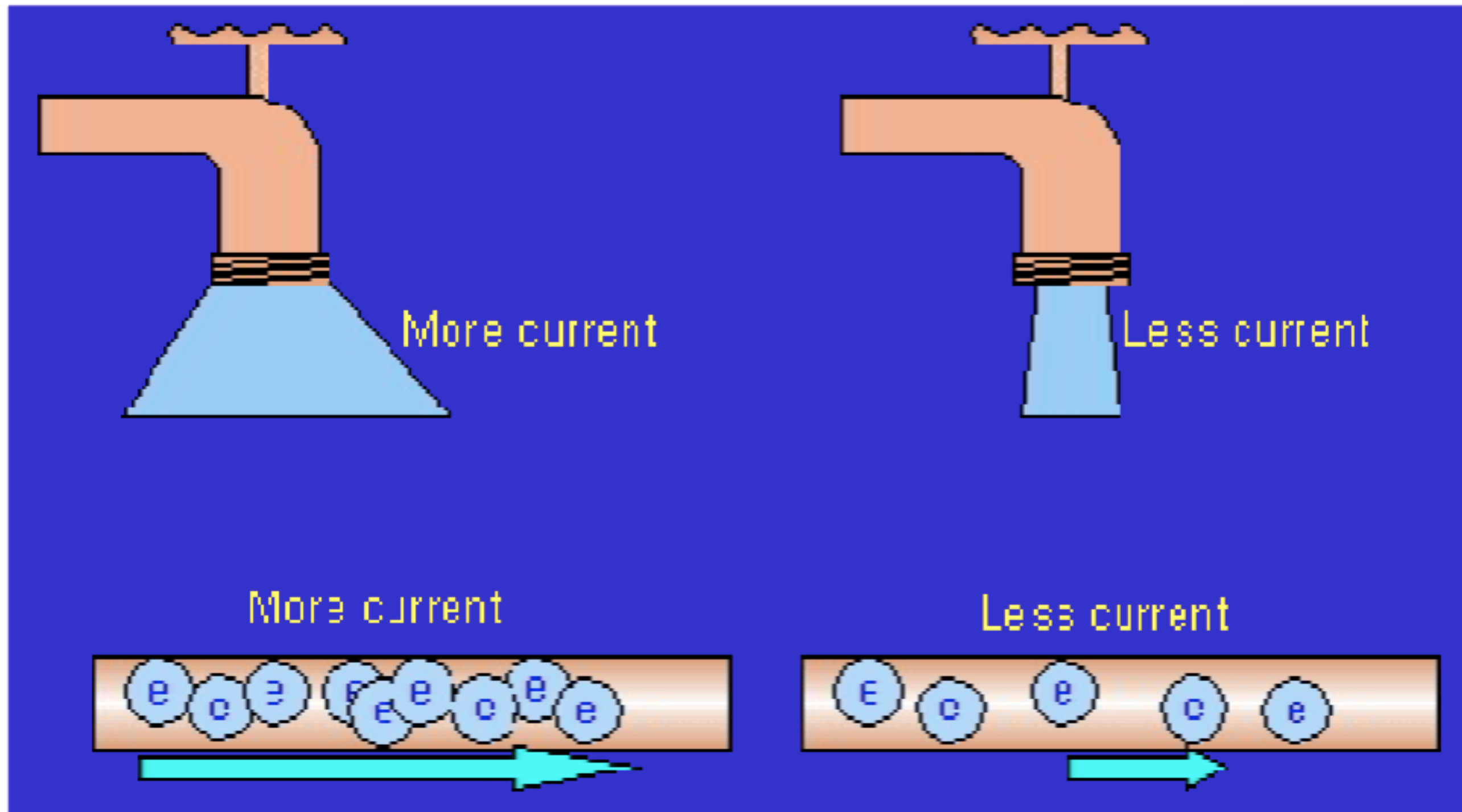


Amperage, Current is often compared to water flow

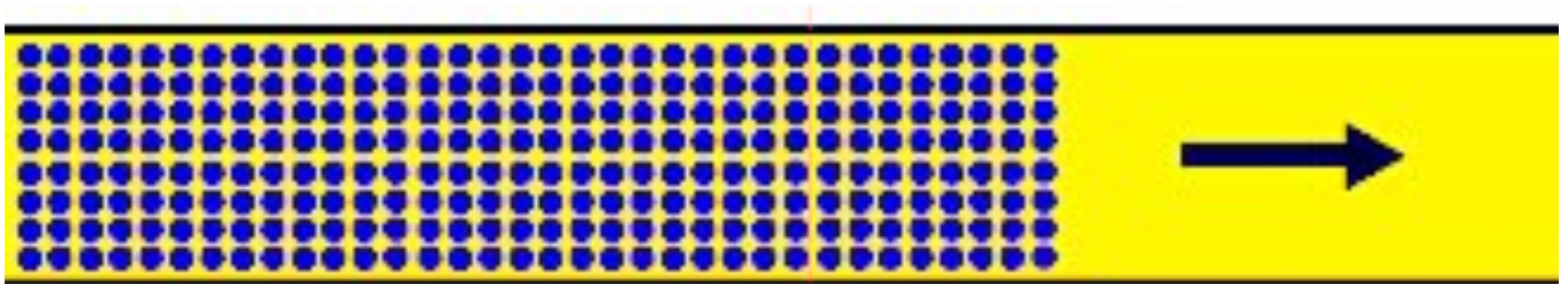
A wire carrying 1 Ampere carries about...



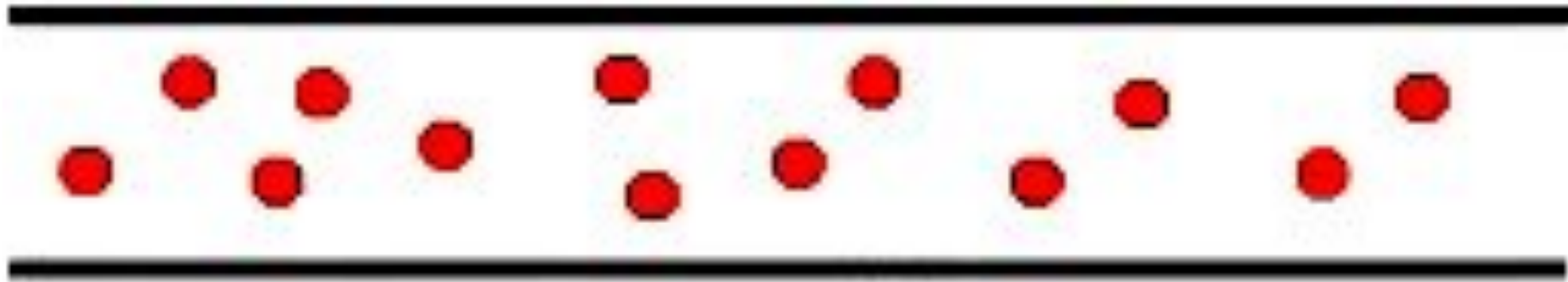6,241,000,000,000,000 electrons across it
per second




Low Amperage= few electrons flowing

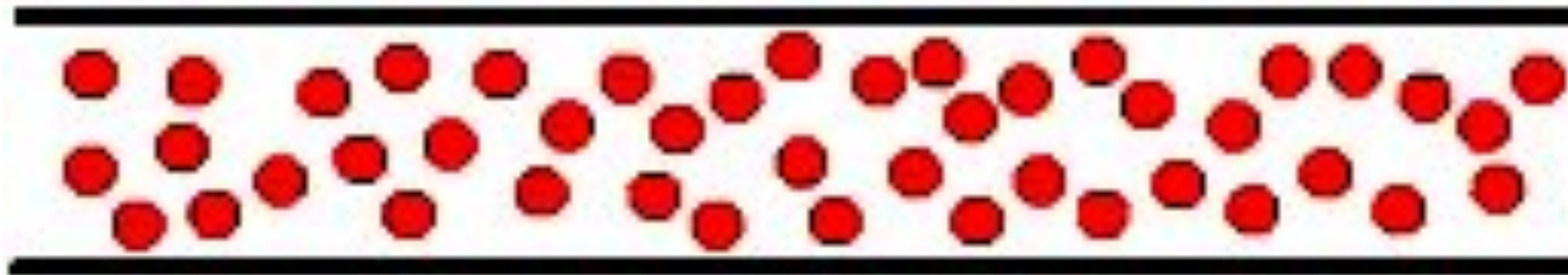


High Amperage= many electrons flowing


Resistance Ω Ohms

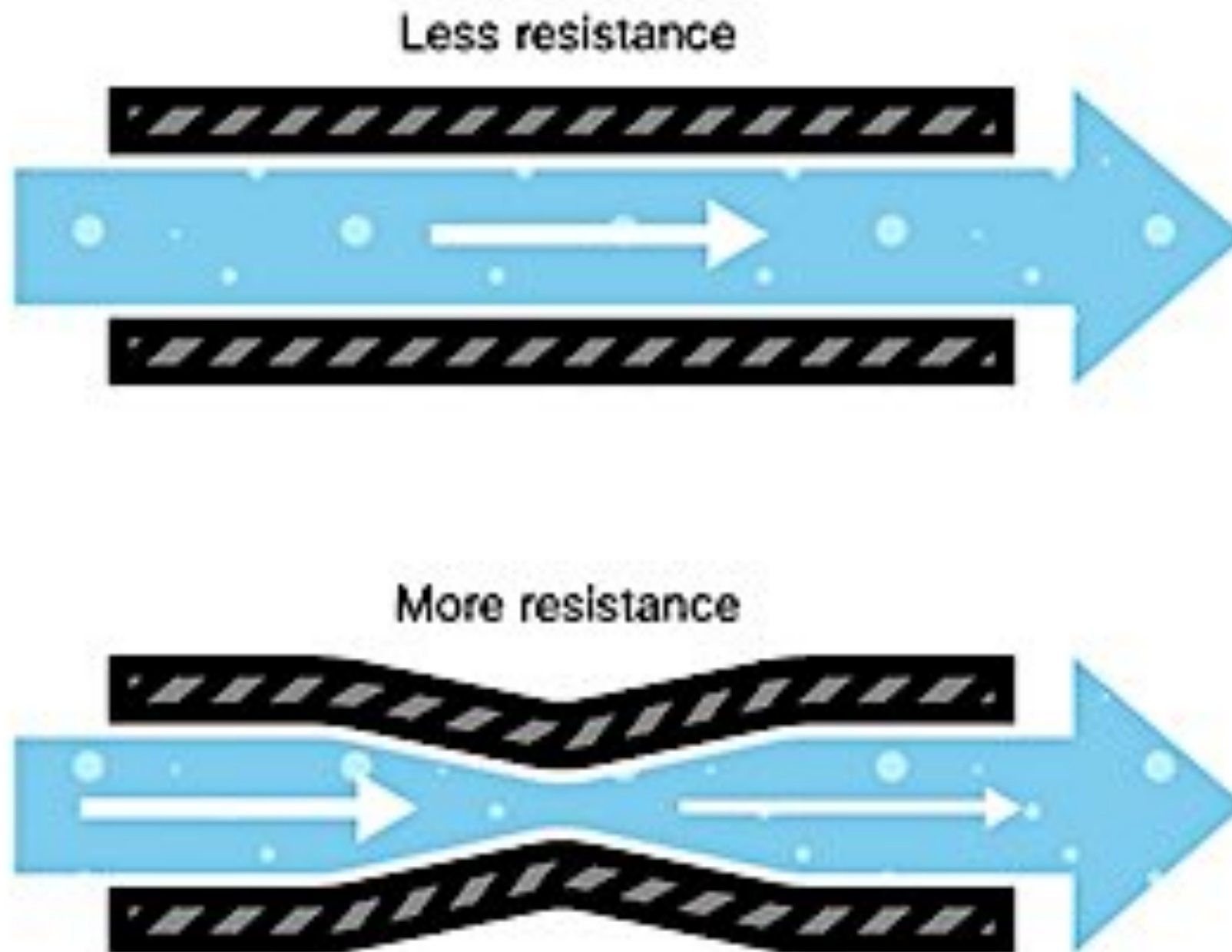

Resistance(R) or Ohms (Ω) is a material's tendency to resist the rate of charge (amperes/current).


Resistance in a Circuit

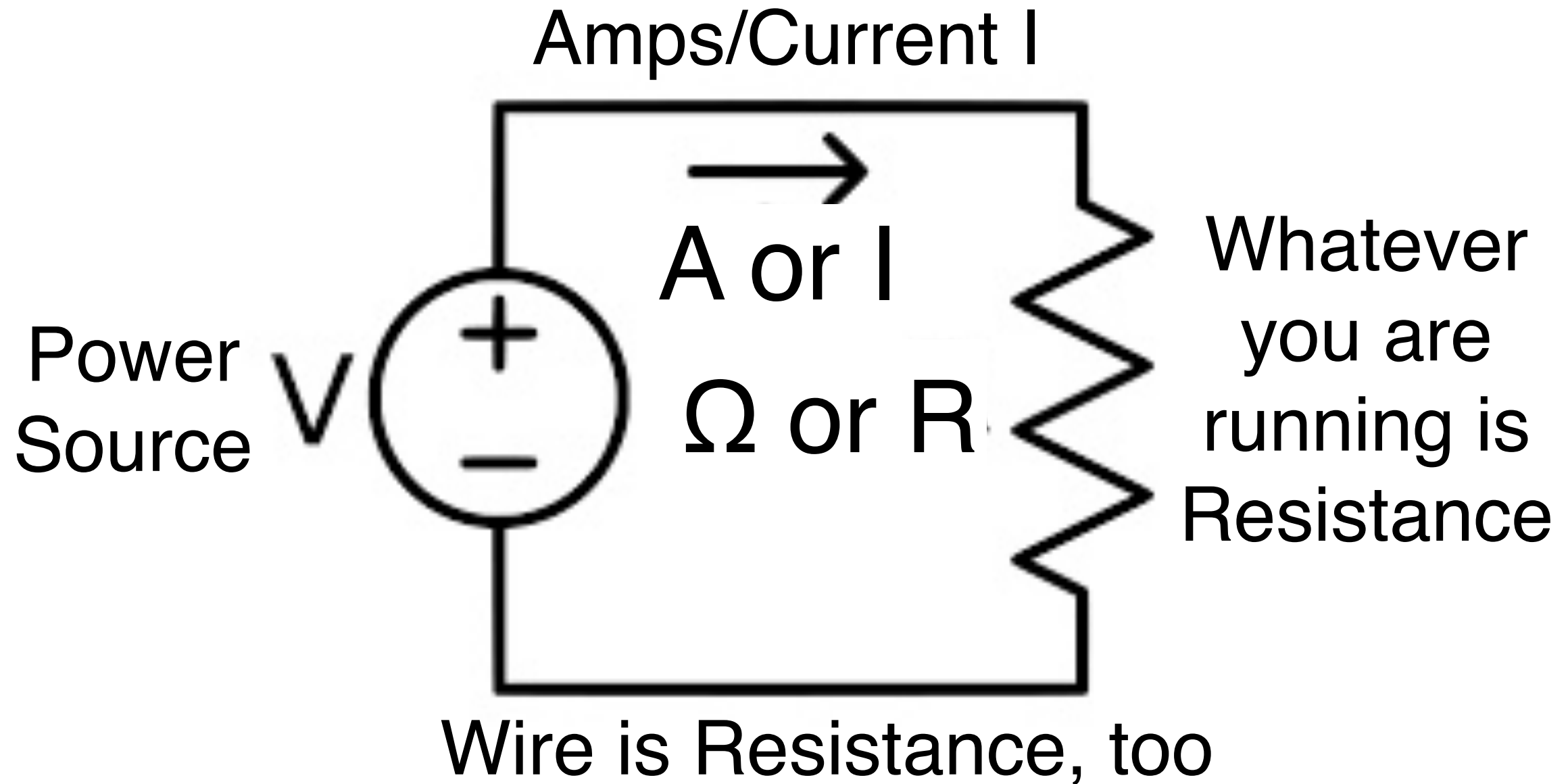

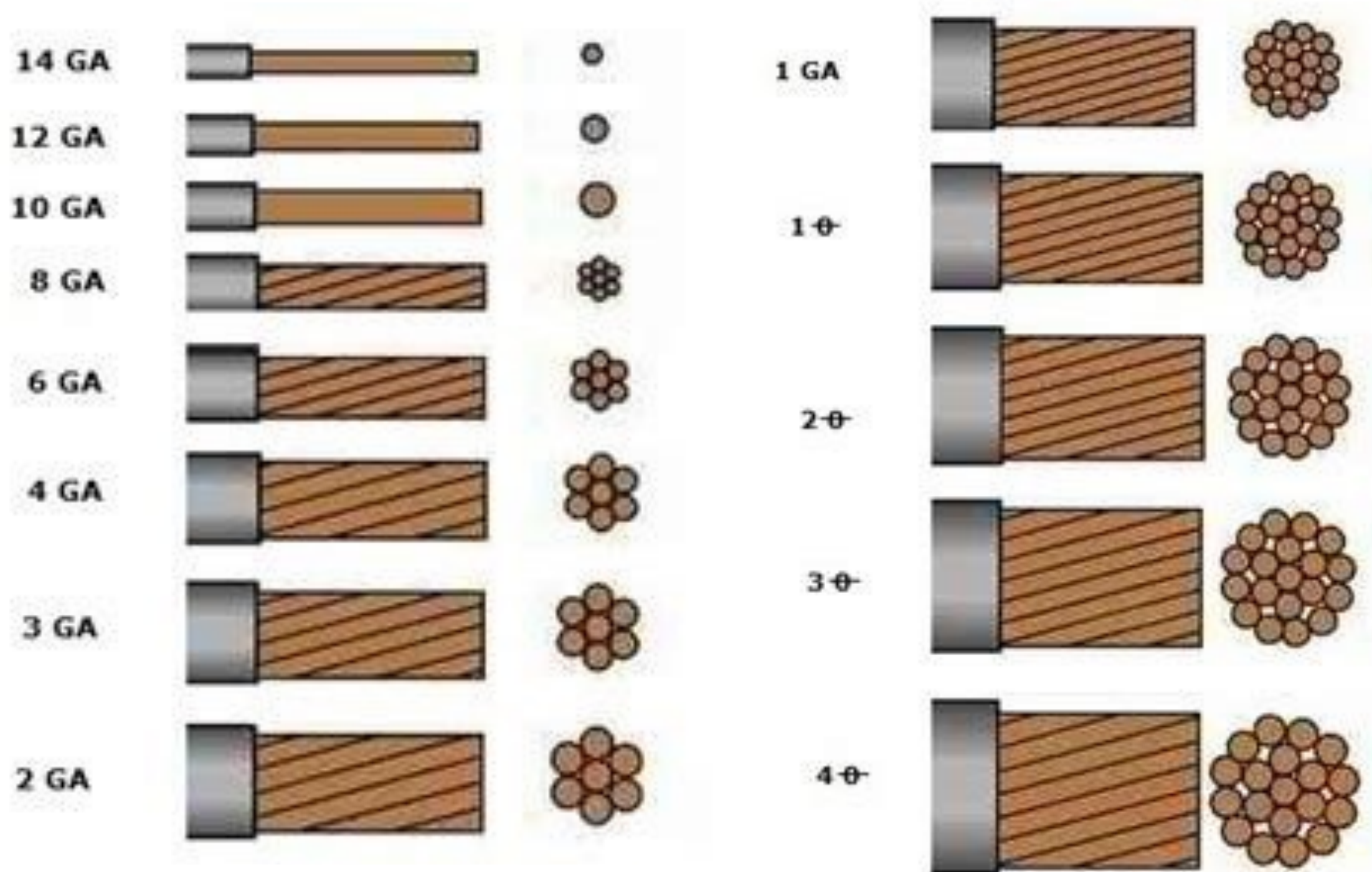


Fatter wires have less Resistance
More available electrons to move


Ohm's Law of Relationships

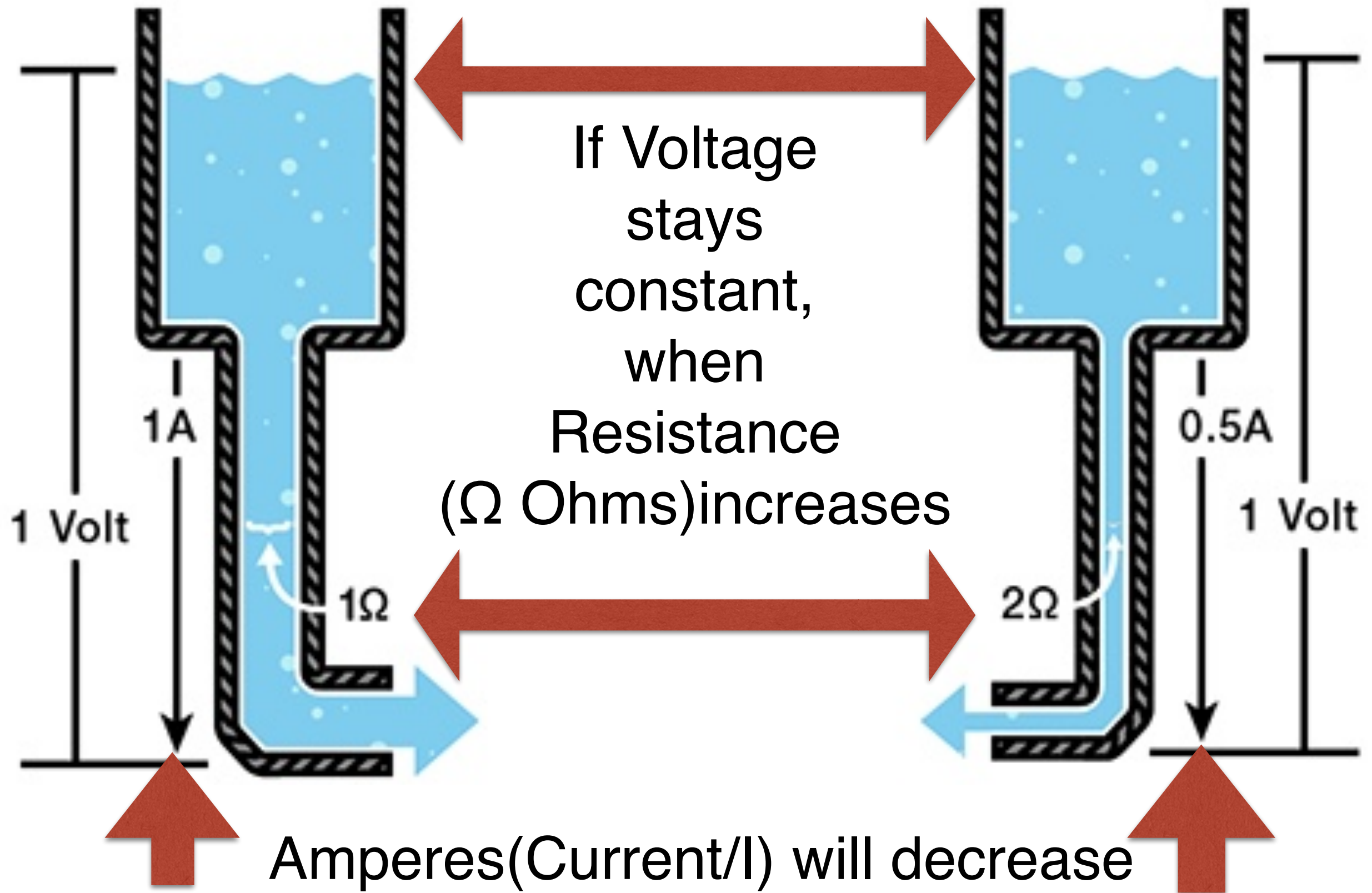

You got Ohm's Law?

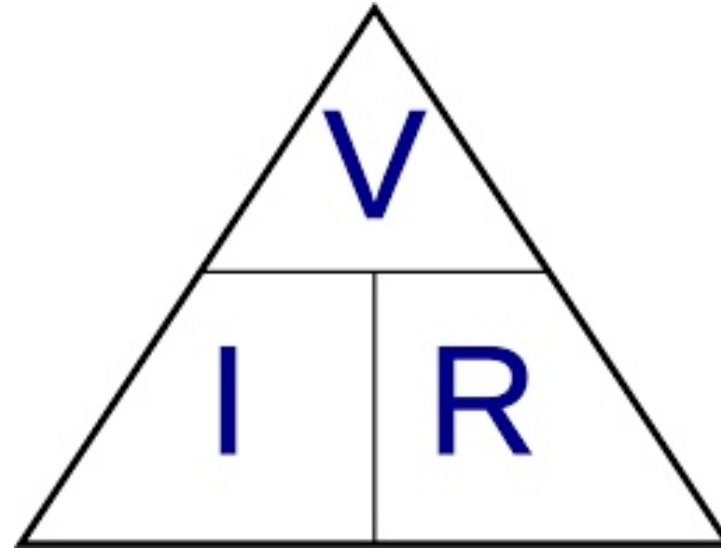


Are you ready for Watt's Law?

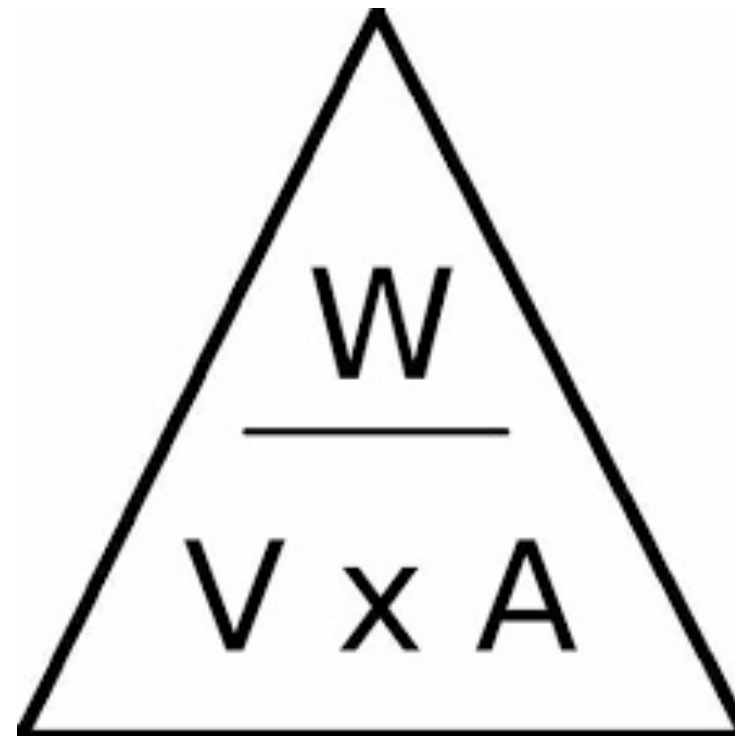

What is a Watt?


Watts Law

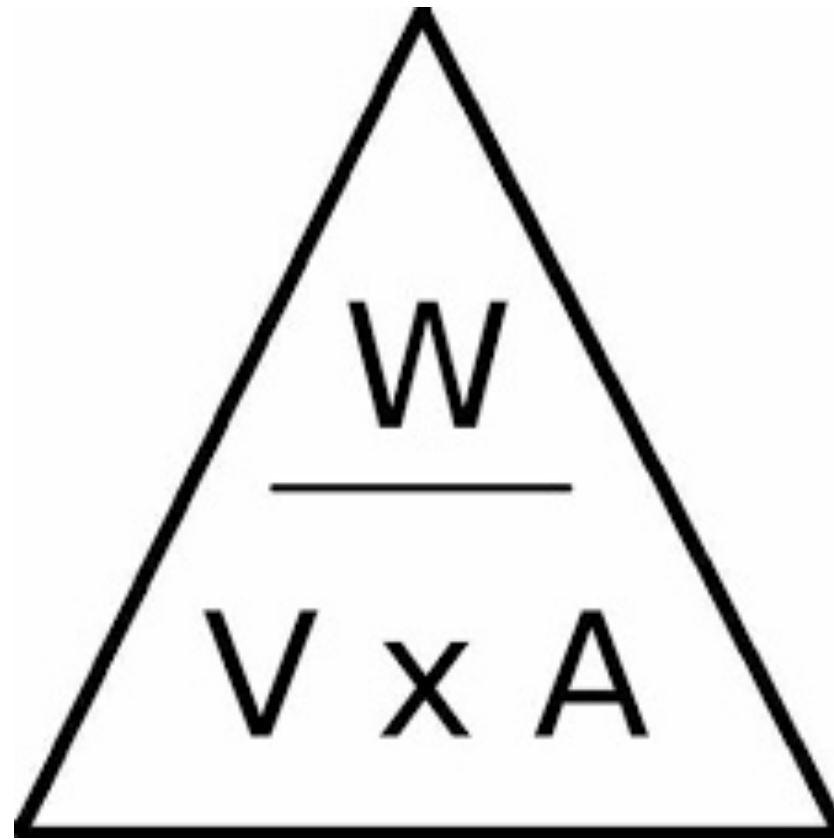


Volts x Amps = Watts

Watts ÷ Amps = Volts

Watts ÷ Volts = Amps

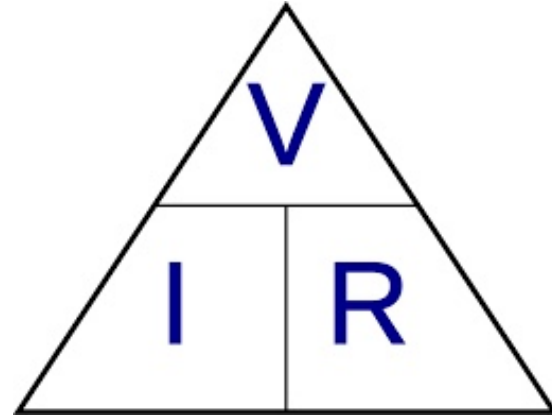


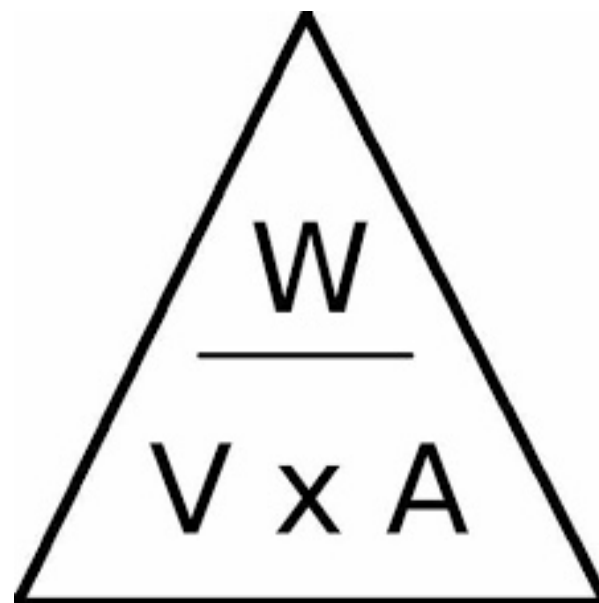Ohm's law defines the relationship between resistance, voltage and current in a circuit.



Watt's law defines the relationship between power, voltage and current.

Watts = Power

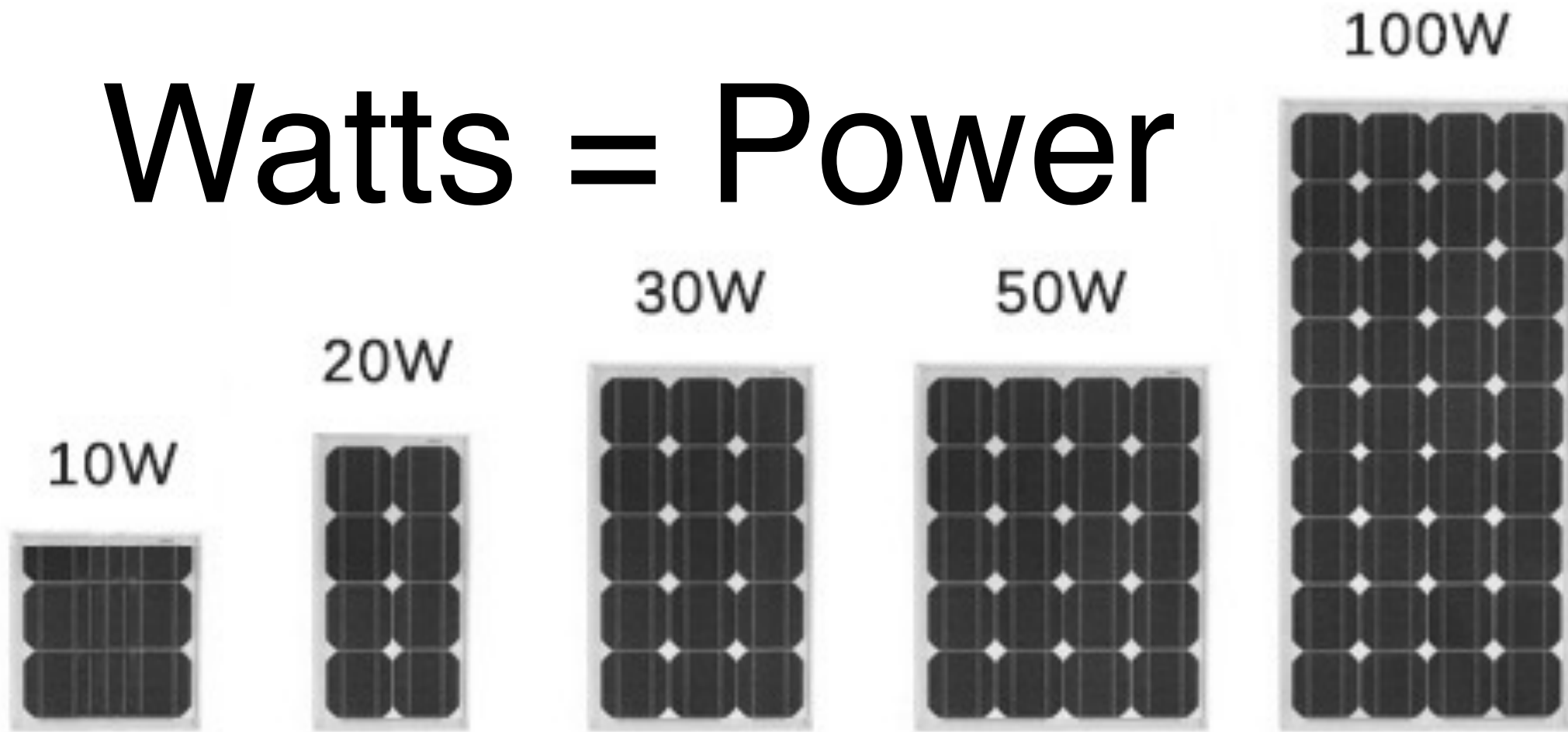


Solar Panels make watts. Appliances use watts



Volts x Amps = Watts

Power producer
Your solar panel

Power user
Food Steamer

windynation www.windynation.com clean power to the people	
100W Polycrystalline Photovoltaic Solar Panel	
Part #:	SOL-100P-01
Maximum Power (Pmax):	100 Watts
Open Circuit Voltage (Voc):	21.60 Volts
Short Circuit Current (Isc):	6.32 Amps
Max Power Voltage (Vpm):	17.40 Volts
Max Power Current (Imp):	5.75 Amps
Max System Voltage:	1000 VDC (600 VDC UL)
Dimensions:	40.0" x 26.4" x 1.2" [1015mm x 670mm x 30mm]
Weight:	18.7 lbs [8.5kg]
Max Series Fuse Rating:	8 Amps
Nom Operating Cell Temp:	48 C [±2]
	

Oster	FOOD STEAMER	
MODEL: 5716		LISTED
120V~, 60Hz, 900W		E 138980
		6K89
DO NOT IMMERSE IN WATER		
NE PAS IMMERGER DANS L'EAU		
FOR HOUSEHOLD USE ONLY		
USAGE DOMESTIQUE SEULEMENT		
MADE IN CHINA / FABRIQUÉ EN CHINE P.N. 124894		

Here you have to
do the math
 $900W \div 120V = 7.5A$

$$17.40V \times 5.75A = 100.05W$$

Power is measured in
Watt Hours (WH),
the number of watts
produced per hour
or used per hour

DC appliances			
Item	Watts	Hours per day	Watt hours
5 Led lights	25	4	100
Phone charger	24	1.5	36
Water pump	40	0.5	20
Speaker system	25	4	100
Fridge	45	4	180
Ceiling fan	25	1	25
Total Watt hours DC			461
AC appliances			
Item	Watts	Hours per day	Watt hours
Laptop charger	50	4	200
Blender	1000	0.03	30
Egg cooker	500	0.16	80
Total Watt hours AC			310
Total Watt hours per day			771



Managing Electricity

As we said...

The movement of electrons can be defined in terms that make it possible to manage electricity.

Series & Parallel


Components can be wired
in **Series** or **Parallel**.

If you want more Volts, wire in series
Amperage stays constant.

If you want more Amps, wire in parallel.
Voltage stays constant.


Panels in Series

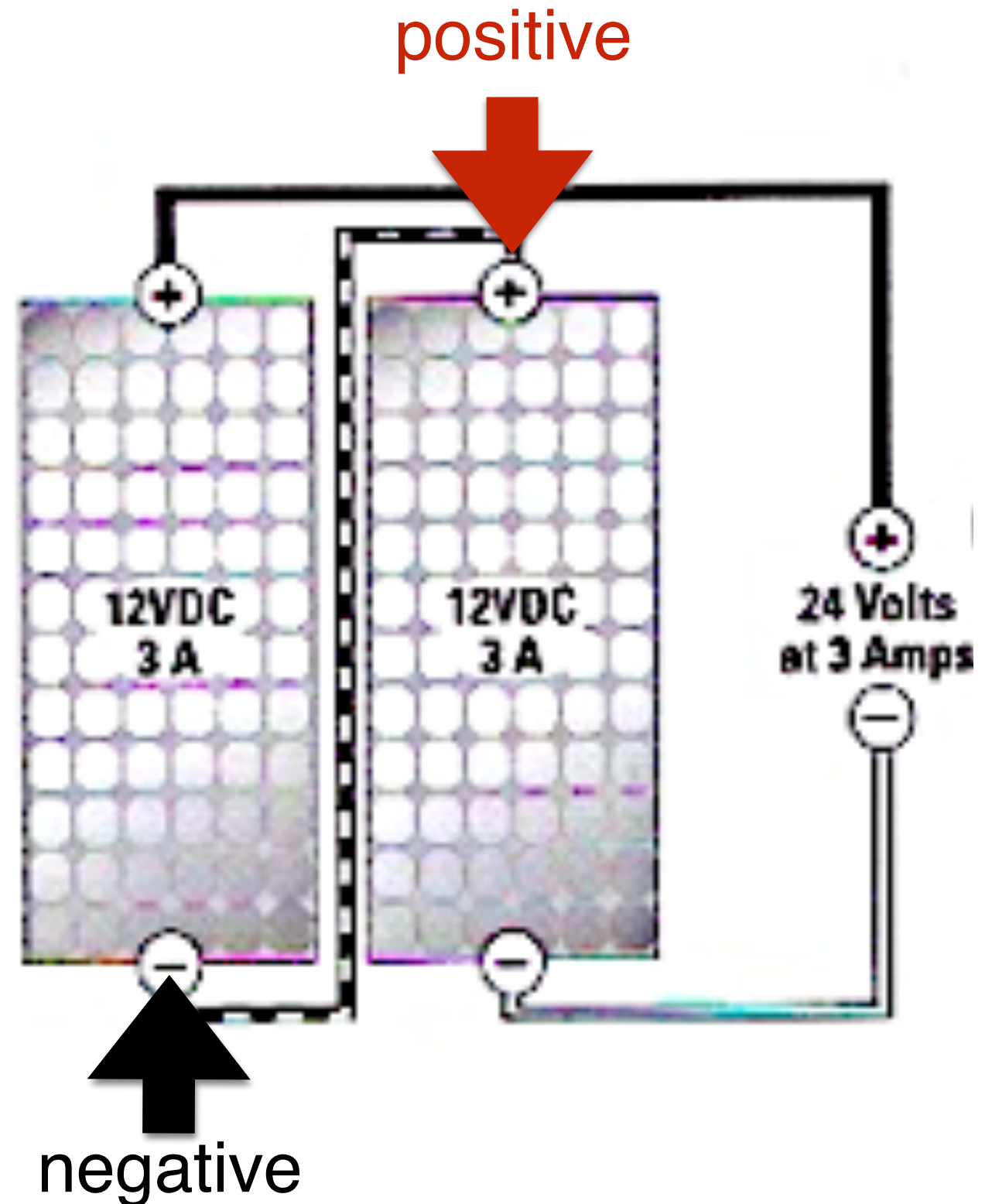Two 12VDC
(12 Volt Direct Current)
Solar Panels in series
wired negative (-)
to **positive (+)**
will produce **24Volts**.
(2 x 12V = 24V)
Amperage stays
constant at 3 Amps




Panels in Parallel

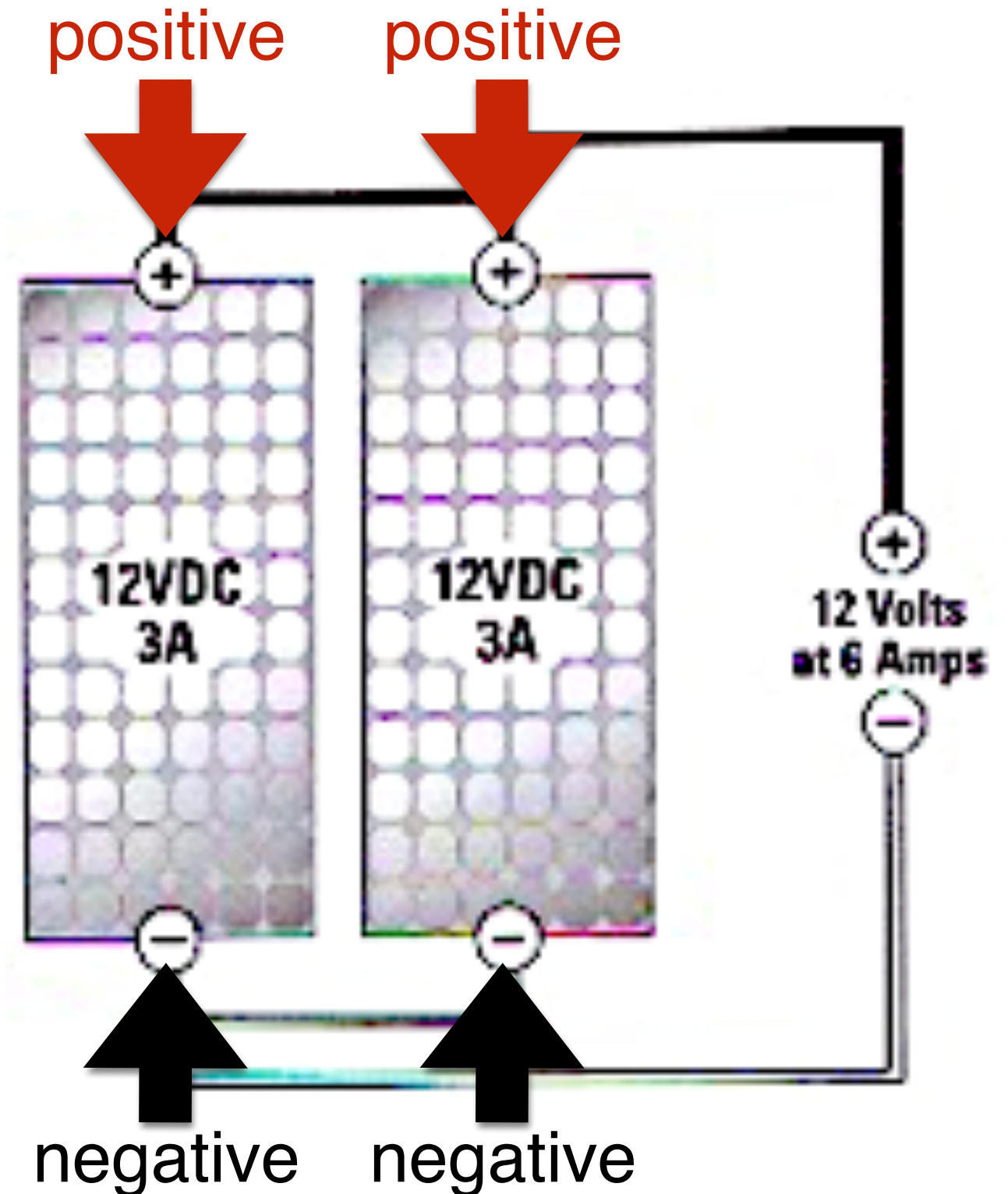
Two 12VDC
(12 Volt Direct Current)
Solar Panels
in parallel wired
negative (-) to negative (-)
positive (+) to positive (+)
will produce **6 Amps**.
($2 \times 3A = 6A$)
Voltage stays
constant at 12V



Series

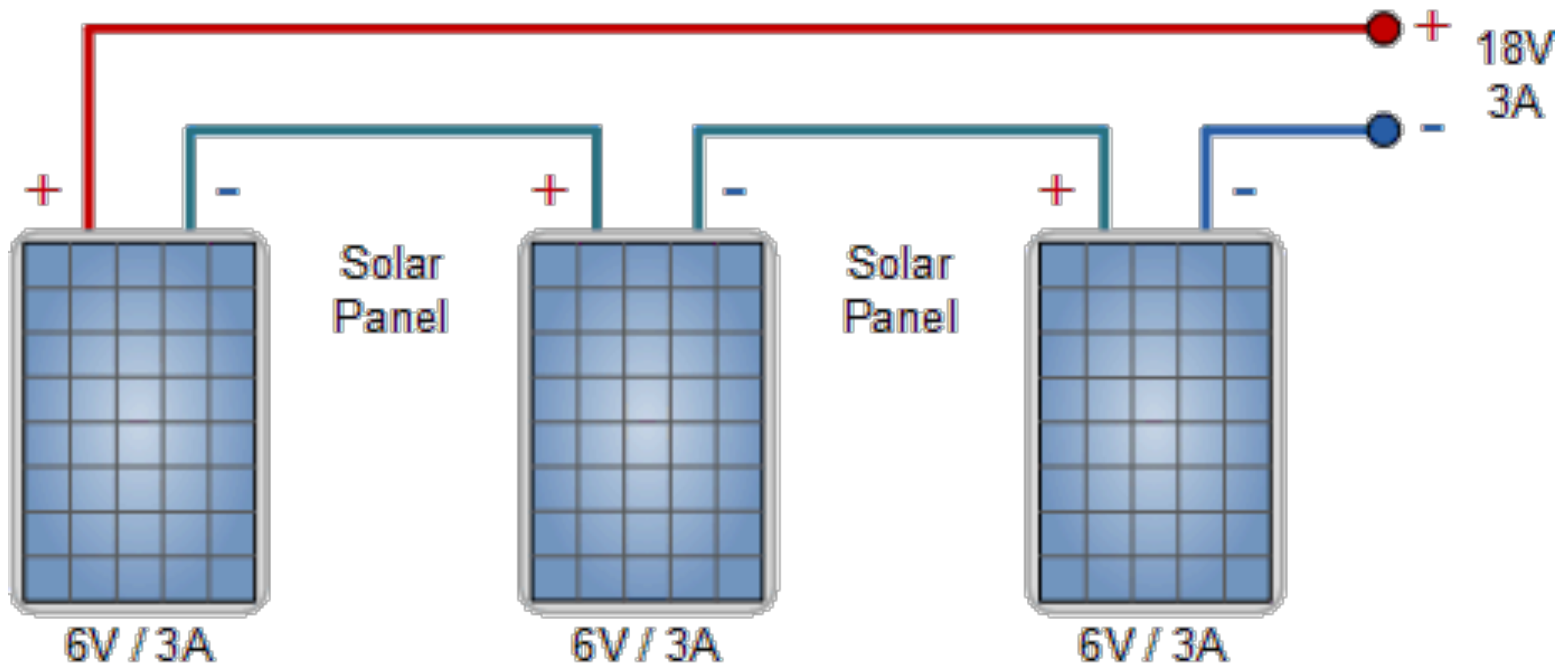


Parallel

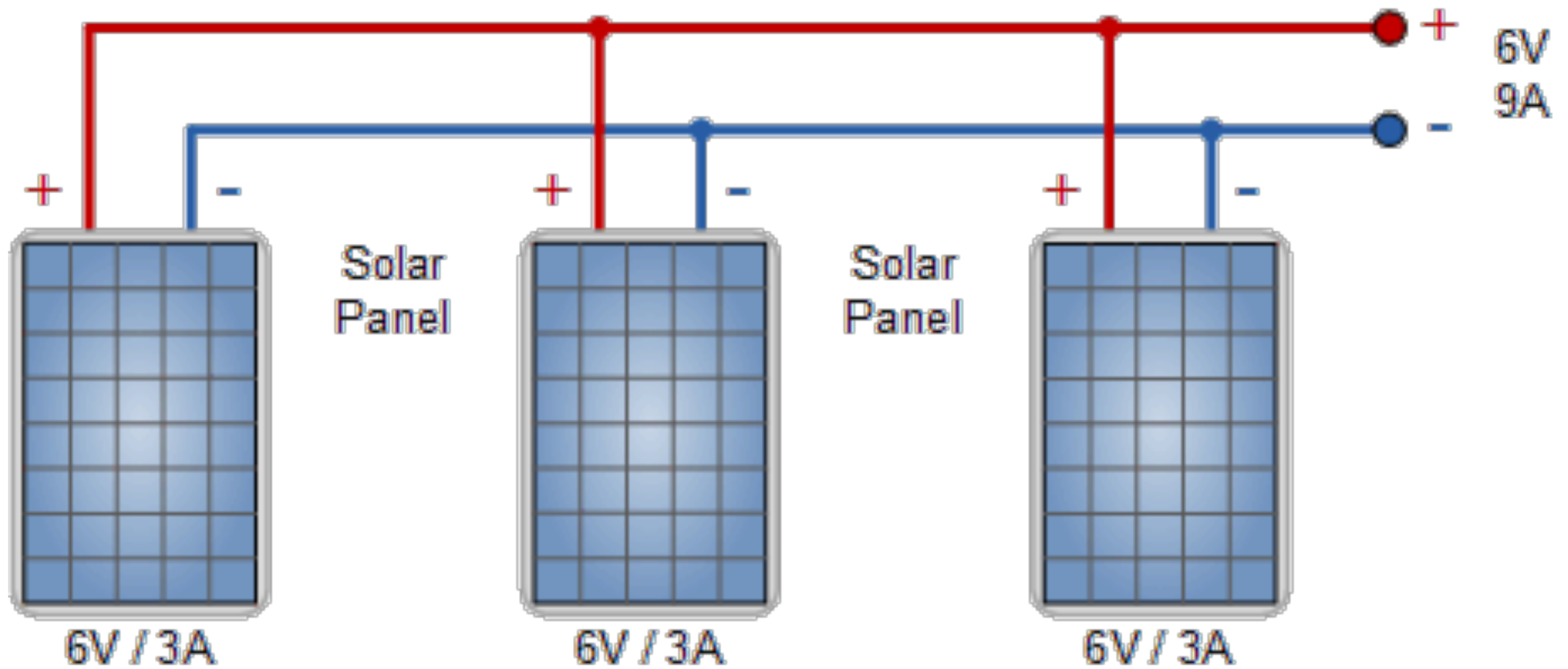

The internal wiring of a solar panel

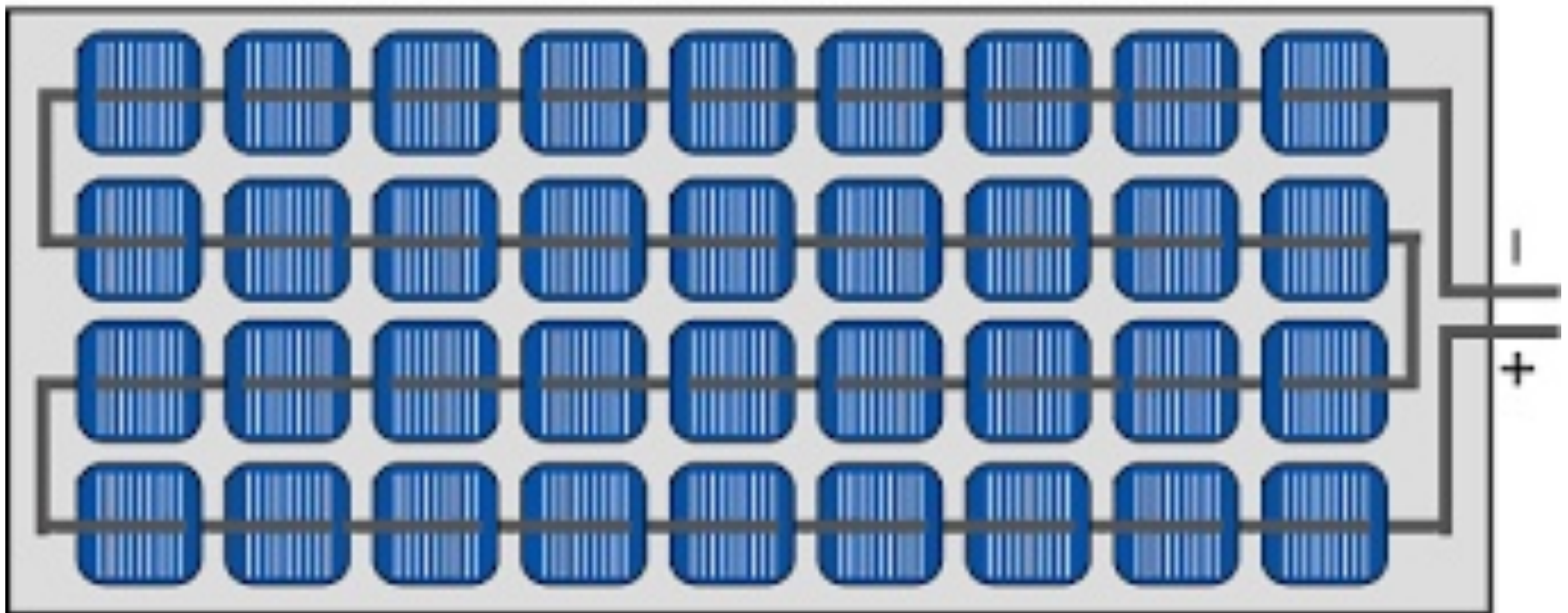A typical module has 36 cells connected in series




One solar cell equals about half a volt (slide #9)
so what is the voltage of this panel?

Batteries can also be wired in
Series and **Parallel**
to boost
Voltage or **Amperage**


Batteries in Series

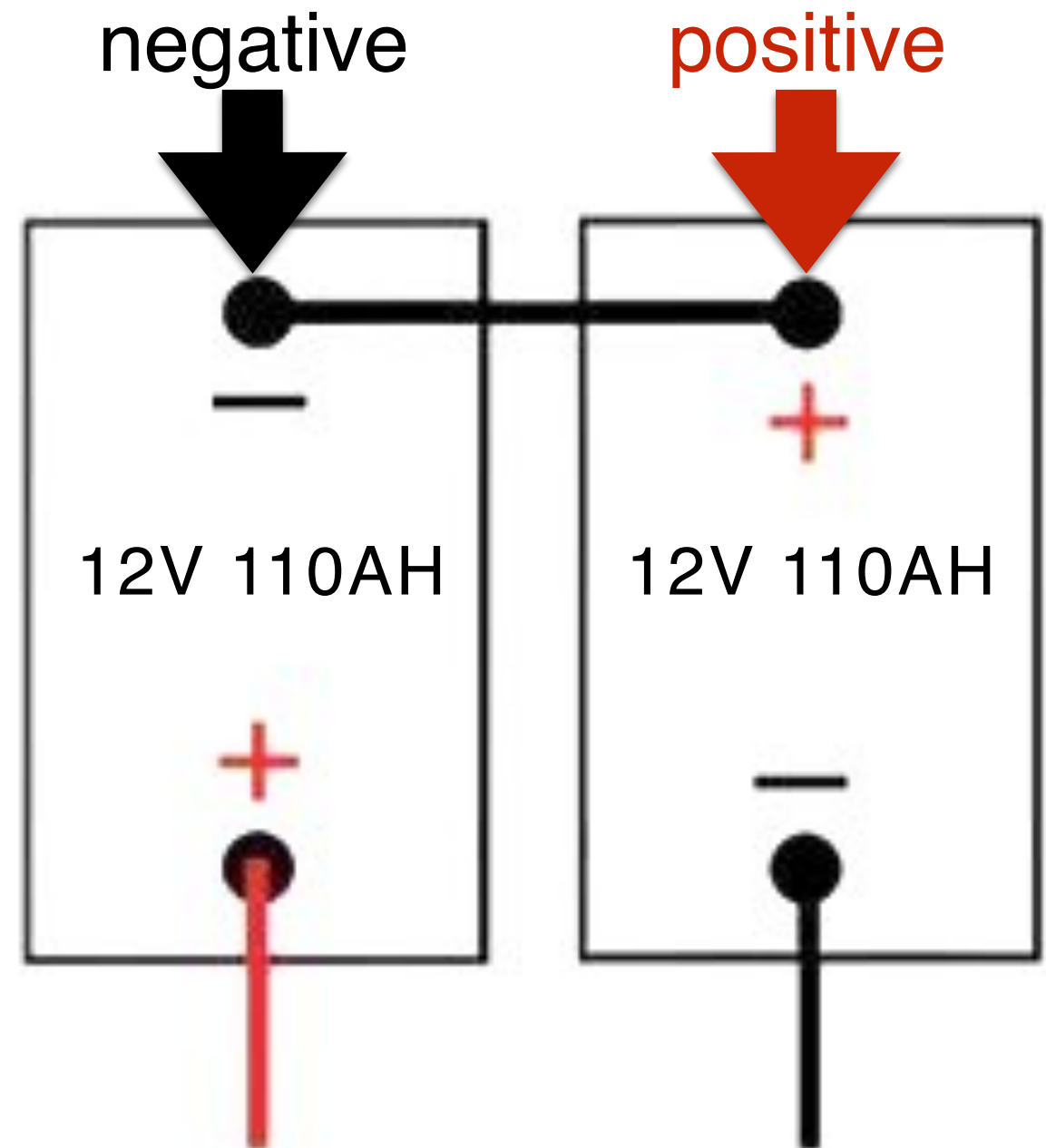Two 12V 110AH
(12 Volt 110 Amp
Hour Batteries)
in series wired
negative (-) to **positive (+)**
will produce
110AH at 24Volts.
Same amperage
twice the voltage.




Batteries in Parallel

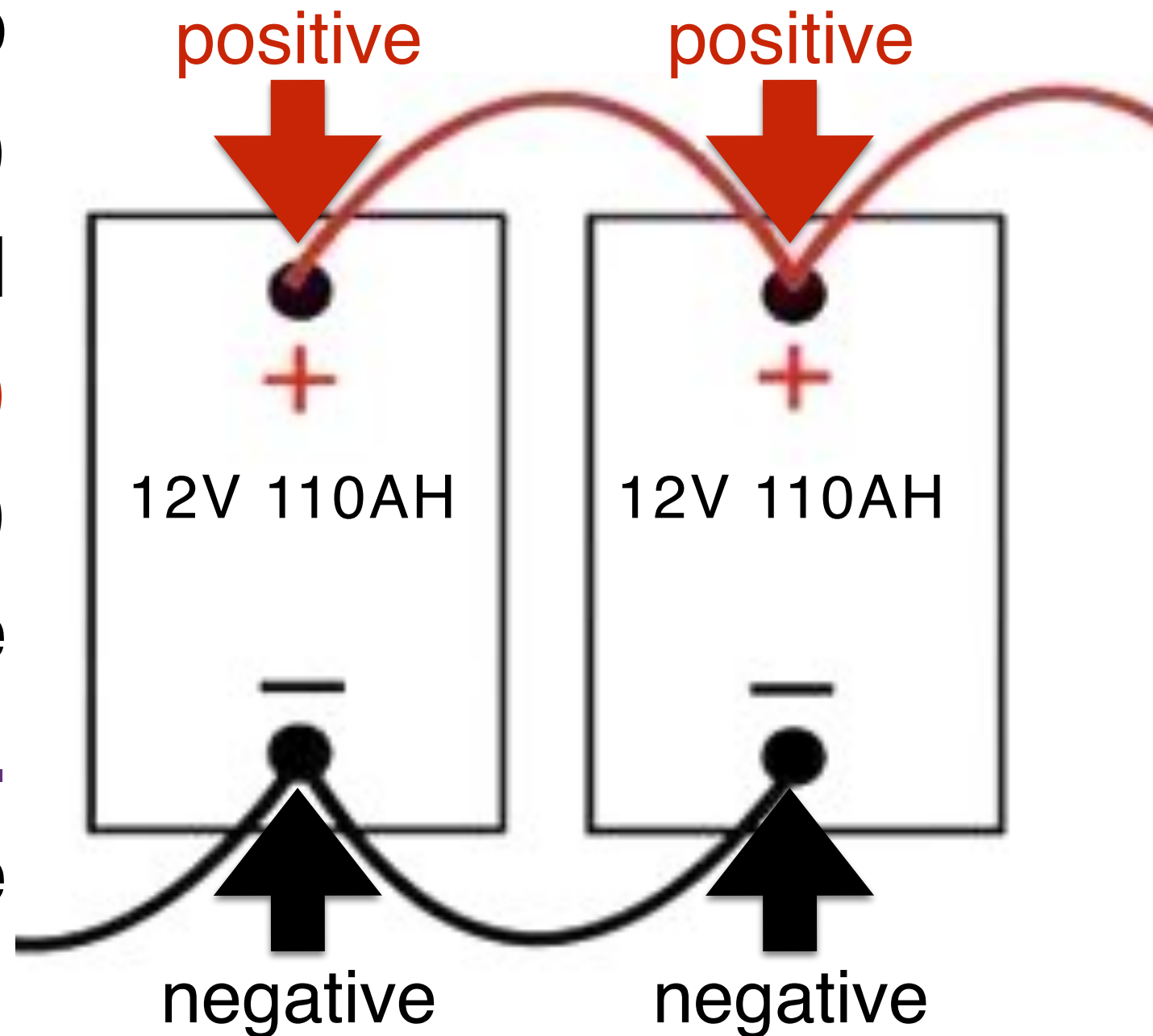Two 12V 110AH
(12 Volt 110 Amp
Hour Batteries)
in parallel wired
positive (+) to positive (+)
negative (-) to negative (-)
will produce
220AH at 12V.
Same voltage
twice the amperage.




Combining Series and Parallel

This is a mind bender

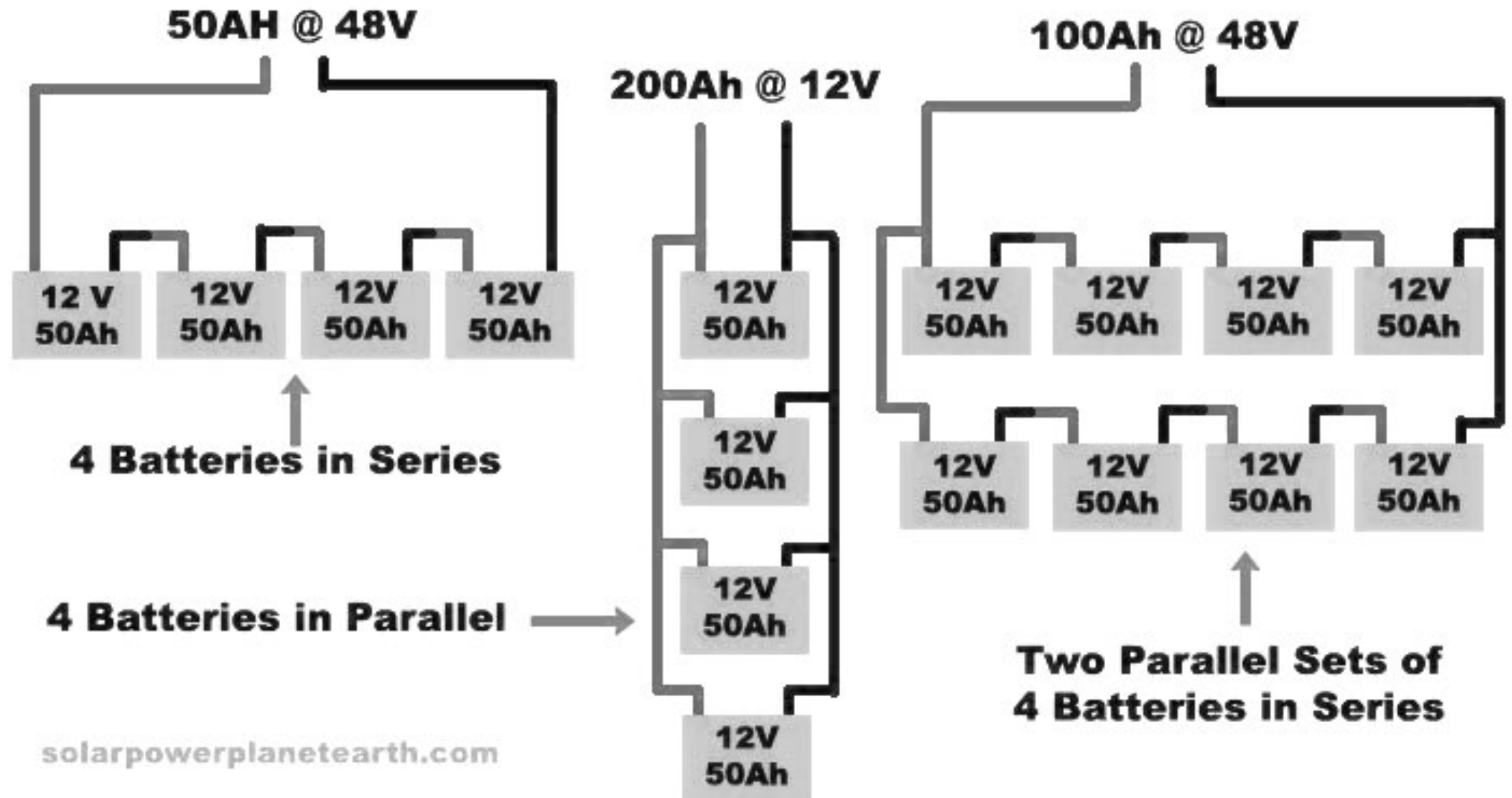


Series Circuits

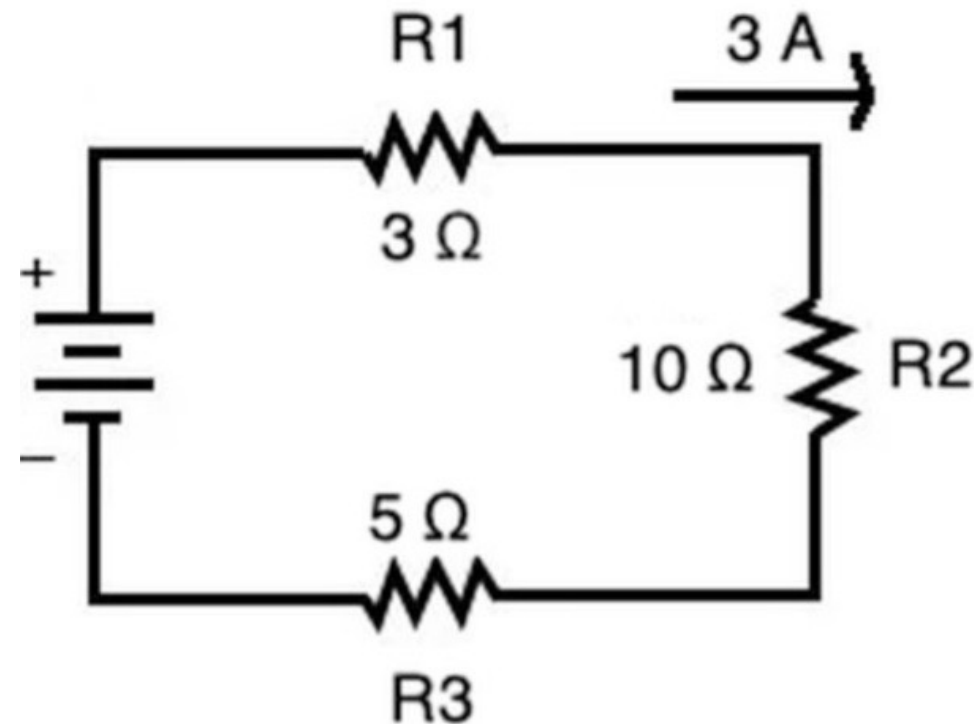

In a series circuit there is only one path for the current to flow. This means current remains constant throughout.


The voltage drops across each resistor according to Ohm's Law $V = IR$.

Parallel Circuits

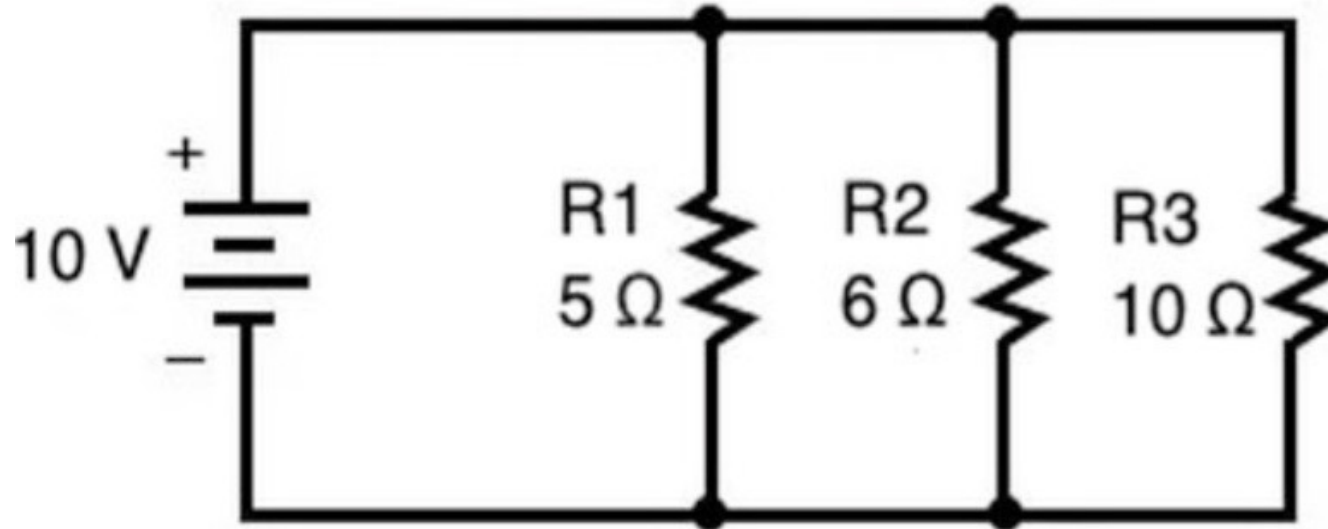


Parallel circuits allow charge to flow through two or more paths. Voltage is the same throughout but amperage varies across the branches with the size of resistor according to Ohms Law, $V=IR$.

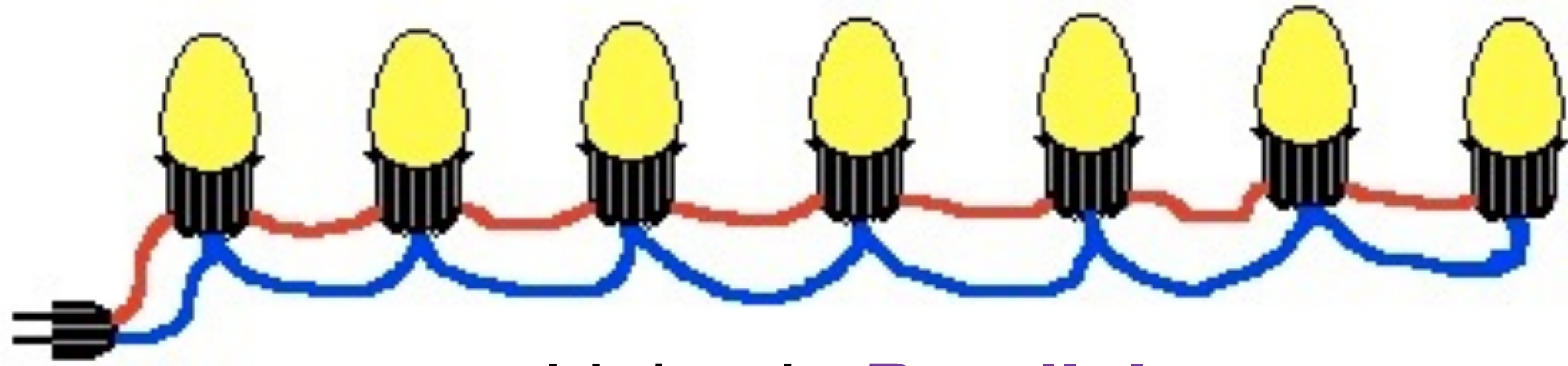Multiple devices are independent of one another so that, if one were to stop working, the others would continue working.



Lights in **Parallel**

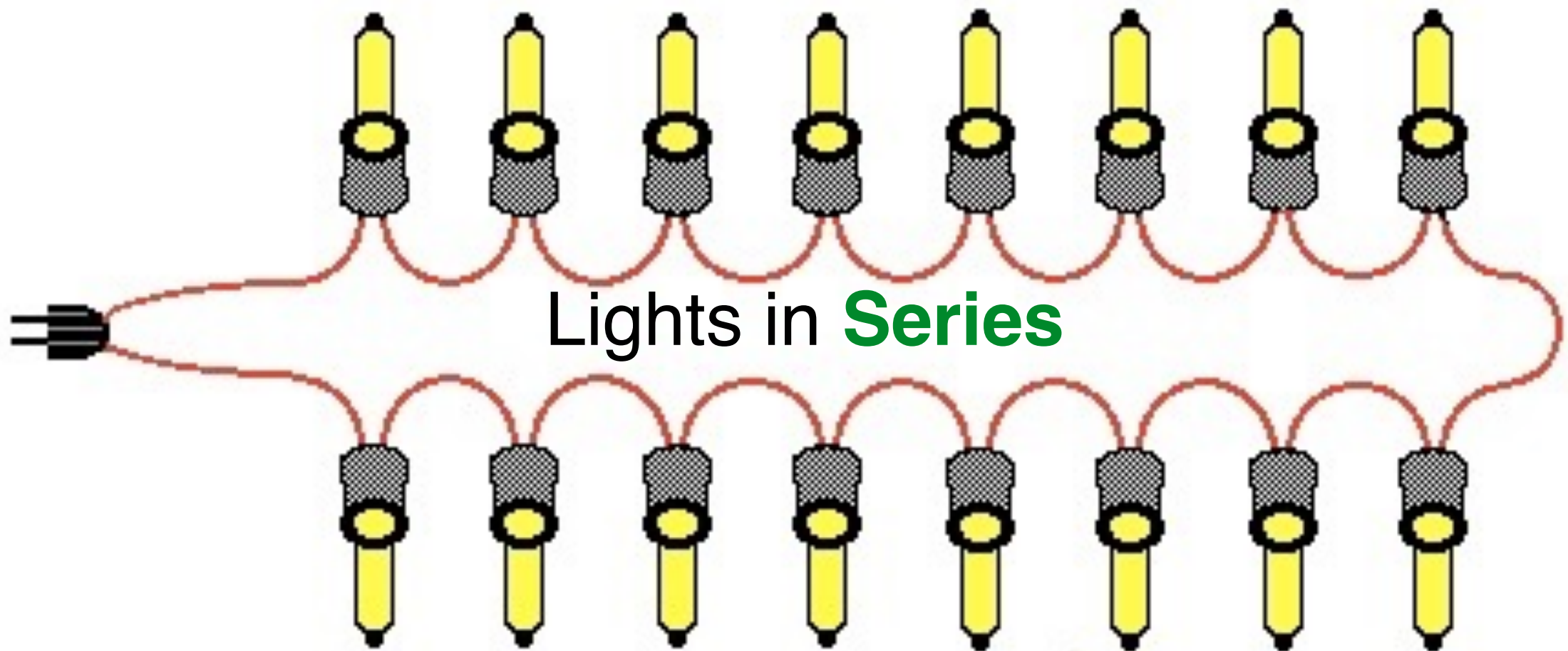

Lights in **Series**

if one light goes out they all go out

Terms for discussion

Electricity

Electrons

Volts

Amps

Current

Ohms

Resistance

Circuit

Charge

Intensité

Ampere

Battery

Amp Hours

Watt Hours

Parallel Wiring

Series Wiring